


Exercise Assignment 12

Brandon Hosley
Mike Davis

Exercise Assignment 12


1. You are stranded on a desert island and you only have NAND gates. Construct the following using only NAND gates. For each of the following show the logic circuit with only NAND gates and the truth table. (Six Points)

Create a NOT gate.

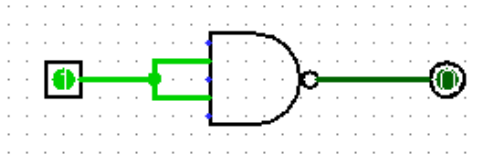


Input	Output
0	1
1	0

Create an AND gate.

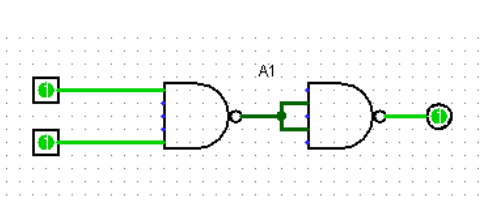


Input			Output
A ₀	B ₀	A ₁	
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

Create an OR gate.

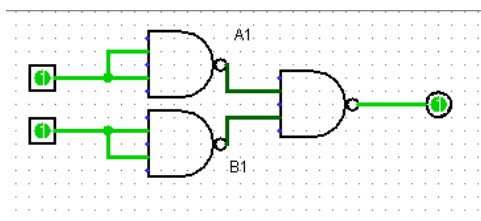


Input				Output
A ₀	B ₀	A ₁	B ₁	
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

Create a NOR gate.

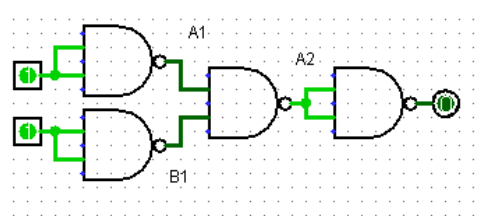


Input					Output
A ₀	B ₀	A ₁	B ₁	A ₂	
0	0	1	1	0	1
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	1	0

Create an XOR gate.

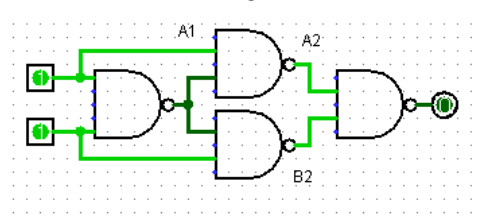

Input					Output
A ₀	B ₀	A ₁	A ₂	B ₂	
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	0

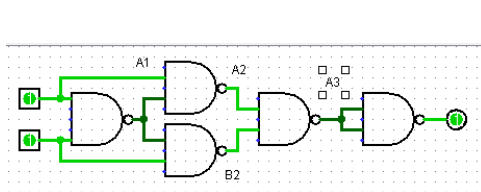
Inverting the output of an XOR gate creates an XNOR gate. Create an XNOR gate.



Input						Output
A ₀	B ₀	A ₁	A ₂	B ₂	A ₃	
0	0	1	1	1	0	1
0	1	1	1	0	1	0
1	0	1	0	1	1	0
1	1	0	1	1	0	1


2. You are stranded on a desert island and you only have NOR gates. Construct the following using only NOR gates. For each of the following, show the logic circuit with only NOR gates and the truth table. (Six Points)

Create a NOT gate.

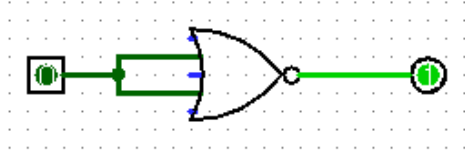


Input		Output
0		1
1		0

Create an AND gate.

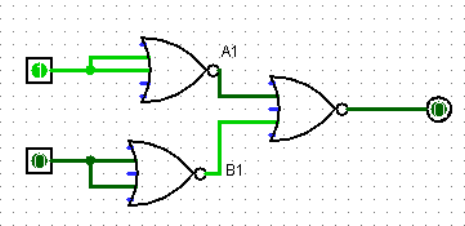


Input				Output
A ₀	B ₀	A ₁	B ₁	
0	0	1	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

Create an OR gate.

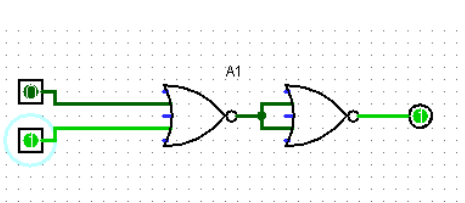


Input			Output
A ₀	B ₀	A ₁	
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

Create a NAND gate.

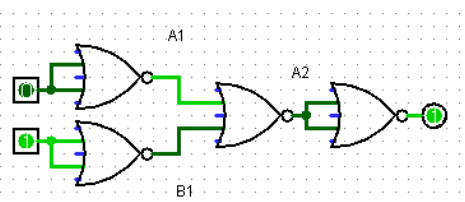


Input					Output
A ₀	B ₀	A ₁	B ₁	A ₂	
0	0	1	1	0	1
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	1	0

Create an XOR gate.

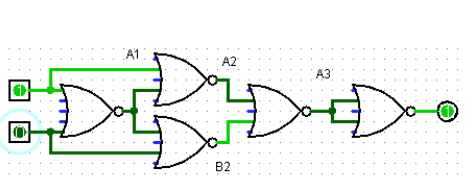

Input						Output
A ₀	B ₀	A ₁	A ₂	B ₂	A ₃	
0	0	1	0	0	1	0
0	1	0	1	0	0	1
1	0	0	0	1	0	1
1	1	0	0	0	1	0

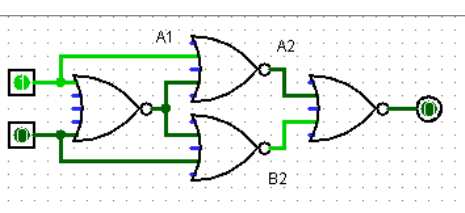Inverting the output of an XOR gate creates an XNOR gate. Create an XNOR gate.



Input					Output
A ₀	B ₀	A ₁	A ₂	B ₂	
0	0	1	0	0	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

References

Warford, J. (2009). *Computer systems* (4th ed.). Jones and Bartlett.